

Precision Temperature-Sensing With RTD Circuits

Author: *Bonnie C. Baker*
Microchip Technology Inc.

INTRODUCTION

The most widely measured phenomena in the process control environment is temperature. Common elements, such as Resistance Temperature Detectors (RTDs), thermistors [7], thermocouples [6] or diodes are used to sense absolute temperatures, as well as changes in temperature. For an overview and comparison of these sensors, refer to Microchip's AN679, "Temperature-Sensing Technologies" [5].

Of these technologies, the platinum RTD temperature-sensing element is the most accurate, linear and stable over time [1] and temperature. RTD element technologies are constantly improving, further enhancing the quality of the temperature measurement. Typically, a data acquisition system conditions the analog signal from the RTD sensor, making the analog translation of the temperature usable in the digital domain.

This application note focuses on circuit solutions that use platinum RTDs in their design (see [Figure 1](#)). The linearity of the RTD will be presented along with standard formulas that can be used to improve the off-the-shelf linearity of the element. For additional information concerning the thermistor temperature sensor, refer to Microchip's AN685, "Thermistors in Single Supply Temperature Sensing Circuits" [7]. Finally, the signal-conditioning path for the RTD system will be covered with application circuits from sensor to microcontroller.

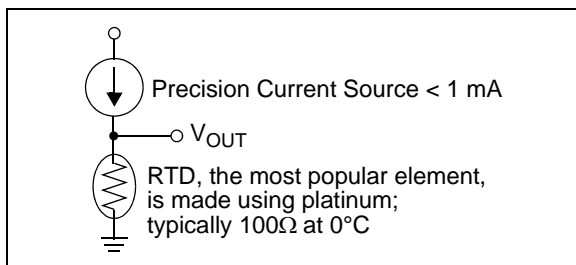


FIGURE 1: RTD Temperature-sensing Elements Use Current Excitation.

RTD OVERVIEW

The acronym "RTD" is derived from the term "Resistance Temperature Detector" [4]. The most stable, linear and repeatable RTD is made of platinum metal. The temperature coefficient of the RTD element is positive and almost constant.

Typical RTD elements are specified with 0°C values of 50, 100, 200, 500, 1000 or 2000 Ω . Of these options, the 100 Ω platinum RTD is the most stable over time and linear over temperature.

The RTD element requires a current excitation. If the magnitude of the current source is too high, the element will dissipate power and start to self-heat. Consequently, care should be taken to insure that less than 1 mA of current is used to excite the RTD element.

An approximation to the platinum RTD resistance change over temperature can be calculated by using the constant $a = 0.00385\Omega/\Omega/^{\circ}\text{C}$ (European curve, ITS-90). This constant is easily used to estimate the absolute resistance of the RTD at temperatures between -100°C and $+200^{\circ}\text{C}$ (with a nominal error smaller than 3.1°C).

EQUATION 1:

$$RTD(T) \approx RTD_0(1 + T \times \alpha)$$

Where:

$RTD(T)$ = the RTD element's resistance at T (Ω),

RTD_0 = the RTD element's resistance at 0°C (Ω),

T = the RTD element's temperature ($^{\circ}\text{C}$),

α = $0.00385 \Omega/\Omega/^{\circ}\text{C}$

If a higher accuracy temperature measurement is required, or a greater temperature range is measured, the standard formula below (Calendar-Van Dusen Equation) can be used in a calculation in the controller engine or be used to generate a look-up table. [Figure 2](#) shows both the RTD resistance and its slope across temperature.

AN687

EQUATION 2:

$$RTD(T) = RTD_0(1 + AT + BT^2 + CT^3(T - 100))$$

Where:

$RTD(T)$ = the RTD element's resistance at T (Ω),

RTD_0 = the RTD element's resistance at 0°C (Ω),

T = the RTD element's temperature ($^\circ\text{C}$) and

A, B, C = are constants derived from resistance measurements at multiple temperatures.

The ITS-90 standard values are:

$RTD_0 = 100\Omega$

$A = 3.9083 \times 10^{-3} \text{ }^\circ\text{C}^{-1}$

$B = -5.775 \times 10^{-7} \text{ }^\circ\text{C}^{-2}$

$C = -4.183 \times 10^{-12} \text{ }^\circ\text{C}^{-4}, \quad T < 0^\circ\text{C}$

$= 0, \quad T \geq 0^\circ\text{C}$

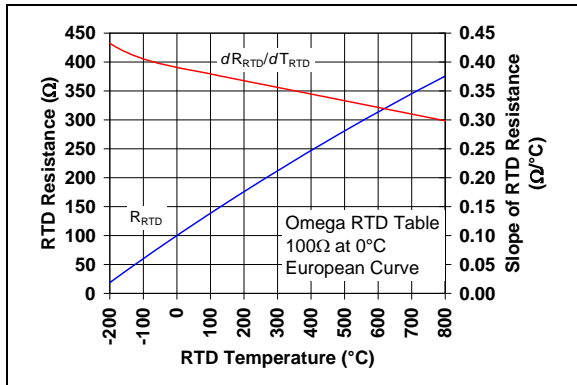


FIGURE 2: The RTD sensing element's temperature characteristic has a positive temperature coefficient that is almost constant.

When the RTD element is excited with a current reference, and self-heating is avoided, the accuracy can be $\pm 4.3^\circ\text{C}$ over the temperature range -200°C to 800°C . The accuracy of a typical RTD is shown in Figure 3.

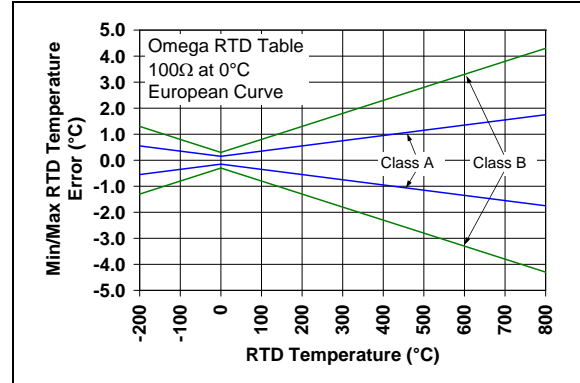


FIGURE 3: The platinum RTD temperature sensor's accuracy is better than other sensors, such as the thermocouple and thermistor.

The advantages and disadvantages of the RTD temperature sensing element is summarized in Table 1.

TABLE 1: RTD TEMPERATURE SENSING ELEMENT ADVANTAGES AND DISADVANTAGES

Advantages	Disadvantages
Very Accurate and Stable	Expensive Solution
Reasonably Linear	Requires Current Excitation
Good Repeatability	Danger of Self-Heating
	Low Resistive Element

RTD CURRENT EXCITATION CIRCUIT

For best linearity, the RTD sensing element requires a stable current reference for excitation. This can be implemented in a number of ways, one of which is shown in Figure 4. In this circuit, a voltage reference, along with two operational amplifiers, are used to generate a floating 1 mA current source.

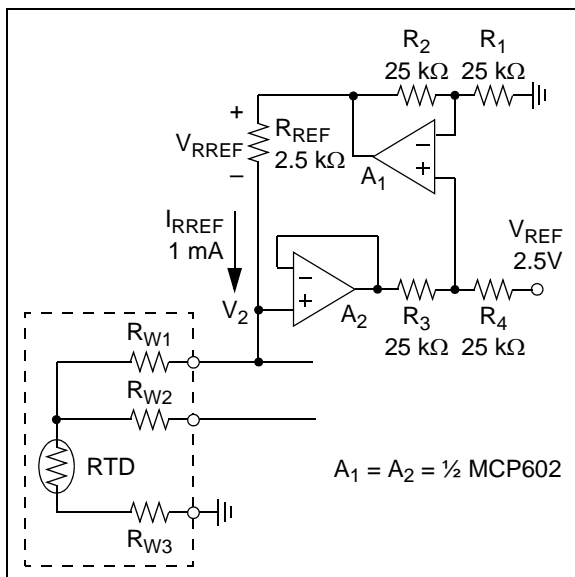


FIGURE 4: A current source for the RTD element can be constructed in a single-supply environment from two op amps and a precision voltage reference.

This is accomplished as follows. The op amp A_1 and the resistors R_1 through R_4 form a difference amplifier with a differential gain (G_{A1}) of 1 V/V (since the resistors are all equal). A 2.5V precision voltage reference (V_{REF}) is applied to the input of this difference amplifier. The output of op amp A_2 ($V_{OUT2} \approx V_2$) serves as the difference amplifier's reference voltage. The voltage at the output of A_1 is shown in Equation 3.

EQUATION 3:

$$V_{OUTA1} = V_{REF}G_{A1} + V_{OUTA2}$$

Where:

$$\begin{aligned} V_{OUTA1} &= A_1\text{'s output voltage} \\ V_{OUTA2} &= A_2\text{'s output voltage} \\ V_{REF} &= \text{Reference voltage at the input} \\ G_{A1} &= \text{Differential Gain} \\ &= 1 \text{ V/V} \end{aligned}$$

Now it is easy to derive the voltage (V_{RREF}) across the resistor R_{REF} , assuming $V_{OUT2} = V_2$; see Equation 4.

EQUATION 4:

$$\begin{aligned} V_{RREF} &= V_{OUTA1} - V_2 \\ V_{RREF} &= V_{REF} \end{aligned}$$

Where:

$$\begin{aligned} V_2 &= \text{Voltage at } A_2\text{'s input} \\ V_{RREF} &= \text{Voltage across } R_{REF} \end{aligned}$$

The current used to bias the RTD assembly (I_{RREF}) is constant and independent of the voltage V_2 (which is across the RTD element); see Equation 5.

EQUATION 5:

$$\begin{aligned} I_{RREF} &= V_{RREF}/R_{REF} \\ I_{RREF} &= 1 \text{ mA} \end{aligned}$$

This current is ratio-metric to the voltage reference. The same voltage reference should be used in other portions of the circuit, such as the analog-to-digital (A/D) converter reference.

Absolute errors in the circuit will occur as a consequence of the reference voltage, the op amp offset voltages, the output swing of A_1 , mismatches between the resistors and the errors in R_{REF} and the RTD element. The temperature drift of these same elements also causes errors; primarily due to the voltage reference, op amp offset drift and the RTD element.

RTD SIGNAL-CONDITIONING PATH

Changes in resistance of the RTD element over temperature are usually digitized through an A/D conversion, as shown in Figure 5. The current excitation circuit (see Figure 4) excites the RTD element. The magnitude of the current source can be

tuned to 1 mA or less by adjusting R_{REF} . The voltage drop across the RTD element is sensed by A_3 , then gained and filtered by A_4 . With this circuit, a 3-wire RTD element is selected. This configuration minimizes errors due to wire resistance and wire resistance drift over temperature.

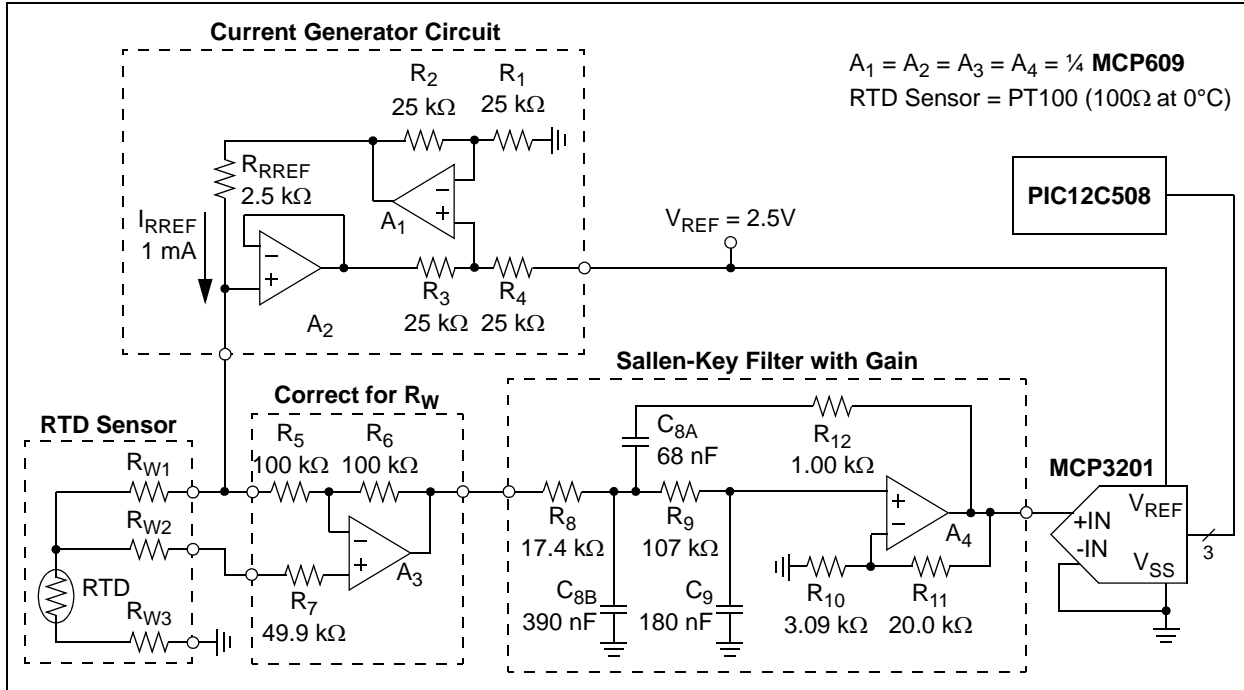


FIGURE 5: This circuit uses a RTD element to measure temperatures from -200°C to 600°C. A current generator excites the sensor. An op amp (A_3) cancels the wire resistance error. Another op amp (A_4) gains and filters the signal. A 12-bit converter (MCP3201) converts the voltage across the RTD to digital code for the 8-pin controller (PIC12C508).

In this circuit, the RTD element equals 100Ω at 0°C. If the RTD is used to sense temperature over the range of -200°C to 600°C, the resistance produced by the RTD would be nominally between 18.5Ω and 313.7Ω, giving a voltage across the RTD between 18.5 mV and 313.7 mV. Since the resistance range is relatively low, wire resistance and wire resistance change over temperature can skew the measurement of the RTD element. Consequently, a 3-wire RTD device is used to reduce these errors.

The errors contributed by the wire resistances, R_{W1} and R_{W3} , are subtracted from the signal with op amp A_3 . In this configuration, R_1 and R_2 are equal and are relatively high. The value of R_1 is selected to ensure that the leakage currents through the resistor do not introduce errors to the current in the RTD element. The transfer function of this portion of the circuit is:

EQUATION 6:

$$V_{OUTA3} = (V_{IN} - V_{W1})(1 + R_6/R_5) - V_{IN}(R_6/R_5)$$

where:

$$V_{IN} = V_{W1} + V_{RTD} + V_{W3}$$

V_{Wx} = the voltage drop across the wires to and from the RTD and

V_{OUTA3} = the voltage at the output of A_3

If nominal resistor values are assumed, then A_3 's output voltage is significantly simplified:

EQUATION 7:

$$V_{OUTA3} = V_{RTD}$$

Where:

$$R_5 = R_6$$

$$R_{W1} = R_{W3}$$

The voltage signal at the output of A_3 is filtered with a 2nd order, low pass filter created with A_4 , R_8 , C_{8A} , C_{8B} , R_9 and C_9 . It is designed to have a Bessel response and a bandwidth of 10 Hz. R_{10} and R_{11} set a gain of 7.47 V/V. It reduces noise and prevents aliasing of higher frequency signals.

This filter uses a Sallen-Key topology specially designed for high gain; see [10]. The capacitor divider formed by C_{8A} and C_{8B} improve this filter's sensitivity to component variations; the filter can be unproducible without this improvement. R_{12} isolates A_4 's output from the capacitive load formed by the series connection of C_{8A} and C_{8B} ; it also improves performance at higher frequencies.

The voltage at A_4 's output is nominally between 0.138V and 2.343V, which is less than V_{REF} (2.5V). The 12-bit A/D converter (MCP3201) gives a nominal temperature resolution of 0.22°C/LSb.

CONCLUSION

Although the RTD requires more circuitry in the signal-conditioning path than the thermistor or the silicon temperature sensor, it ultimately provides a high-precision, relatively accurate result over a wider temperature range.

If this circuit is properly calibrated, and temperature correction coefficients are stored in the PIC, it can achieve $\pm 0.01^\circ\text{C}$ accuracy.

REFERENCES

RTD Temperature Sensors

- [1] "Evaluating Thin Film RTD Stability", SENSORS, Hyde, Darrell, Oct. 1997, pg. 79.
- [2] "Refresher on Resistance Temperature Devices", Madden, J.R., SENSORS, Sept. 1997, pg. 66.
- [3] "Producing Higher Accuracy From SPRTs (Standard Platinum Resistance Thermometer)", MEASUREMENT & CONTROL, Li, Xumo, June 1996, pg. 118.
- [4] "Practical Temperature Measurements", OMEGA[®] Temperature Measurement Handbook, The OMEGA[®] Made in the USA Handbook[™], Vol. 1, pp. Z-33 to Z-36 and Z-251 to Z-254.

Other Temperature Sensors

- [5] AN679, "Temperature Sensing Technologies", DS00679, Baker, Bonnie, Microchip Technology Inc.
- [6] AN684, "Single-Supply Temperature Sensing with Thermocouples", DS00684, Baker, Bonnie, Microchip Technology Inc.
- [7] AN685, "Thermistors in Single-Supply Temperature-Sensing Circuits", DS00685, Baker, Bonnie, Microchip Technology Inc.

Sensor Conditioning Circuits

- [8] AN682, "Using Operational Amplifiers for Analog Gain in Embedded System Design", DS00682, Baker, Bonnie, Microchip Technology Inc.
- [9] AN990, "Analog Sensor Conditioning Circuits – An Overview," DS00990, Kumen Blake, Microchip Technology Inc.

Active Filters

- [10] Kumen Blake, "Transmit Filter Handles ADSL Modem Tasks," Electronic Design, June 28, 1999.

AN687

NOTES:

Note the following details of the code protection feature on Microchip devices:

- Microchip products meet the specification contained in their particular Microchip Data Sheet.
- Microchip believes that its family of products is one of the most secure families of its kind on the market today, when used in the intended manner and under normal conditions.
- There are dishonest and possibly illegal methods used to breach the code protection feature. All of these methods, to our knowledge, require using the Microchip products in a manner outside the operating specifications contained in Microchip's Data Sheets. Most likely, the person doing so is engaged in theft of intellectual property.
- Microchip is willing to work with the customer who is concerned about the integrity of their code.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of their code. Code protection does not mean that we are guaranteeing the product as “unbreakable.”

Code protection is constantly evolving. We at Microchip are committed to continuously improving the code protection features of our products. Attempts to break Microchip's code protection feature may be a violation of the Digital Millennium Copyright Act. If such acts allow unauthorized access to your software or other copyrighted work, you may have a right to sue for relief under that Act.

Information contained in this publication regarding device applications and the like is provided only for your convenience and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. MICROCHIP MAKES NO REPRESENTATIONS OR WARRANTIES OF ANY KIND WHETHER EXPRESS OR IMPLIED, WRITTEN OR ORAL, STATUTORY OR OTHERWISE, RELATED TO THE INFORMATION, INCLUDING BUT NOT LIMITED TO ITS CONDITION, QUALITY, PERFORMANCE, MERCHANTABILITY OR FITNESS FOR PURPOSE. Microchip disclaims all liability arising from this information and its use. Use of Microchip devices in life support and/or safety applications is entirely at the buyer's risk, and the buyer agrees to defend, indemnify and hold harmless Microchip from any and all damages, claims, suits, or expenses resulting from such use. No licenses are conveyed, implicitly or otherwise, under any Microchip intellectual property rights.

Trademarks

The Microchip name and logo, the Microchip logo, Accuron, dsPIC, KEELOQ, KEELOQ logo, MPLAB, PIC, PICmicro, PICSTART, rfPIC, SmartShunt and UNI/O are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

FilterLab, Linear Active Thermistor, MXDEV, MXLAB, SEEVAL, SmartSensor and The Embedded Control Solutions Company are registered trademarks of Microchip Technology Incorporated in the U.S.A.

Analog-for-the-Digital Age, Application Maestro, CodeGuard, dsPICDEM, dsPICDEM.net, dsPICworks, dsSPEAK, ECAN, ECONOMONITOR, FanSense, In-Circuit Serial Programming, ICSP, ICEPIC, Mindi, MiWi, MPASM, MPLAB Certified logo, MPLIB, MPLINK, mTouch, PICkit, PICDEM, PICDEM.net, PICtail, PIC³² logo, PowerCal, PowerInfo, PowerMate, PowerTool, REAL ICE, rfLAB, Select Mode, Total Endurance, WiperLock and ZENA are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

SQTP is a service mark of Microchip Technology Incorporated in the U.S.A.

All other trademarks mentioned herein are property of their respective companies.

© 2008, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.

 Printed on recycled paper.

QUALITY MANAGEMENT SYSTEM
CERTIFIED BY DNV
== ISO/TS 16949:2002 ==

Microchip received ISO/TS-16949:2002 certification for its worldwide headquarters, design and wafer fabrication facilities in Chandler and Tempe, Arizona; Gresham, Oregon and design centers in California and India. The Company's quality system processes and procedures are for its PIC® MCUs and dsPIC® DSCs, KEELOQ® code hopping devices, Serial EEPROMs, microperipherals, nonvolatile memory and analog products. In addition, Microchip's quality system for the design and manufacture of development systems is ISO 9001:2000 certified.



WORLDWIDE SALES AND SERVICE

AMERICAS

Corporate Office

2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-792-7200
Fax: 480-792-7277
Technical Support:
<http://support.microchip.com>
Web Address:
www.microchip.com

Atlanta

Duluth, GA
Tel: 678-957-9614
Fax: 678-957-1455

Boston

Westborough, MA
Tel: 774-760-0087
Fax: 774-760-0088

Chicago

Itasca, IL
Tel: 630-285-0071
Fax: 630-285-0075

Dallas

Addison, TX
Tel: 972-818-7423
Fax: 972-818-2924

Detroit

Farmington Hills, MI
Tel: 248-538-2250
Fax: 248-538-2260

Kokomo

Kokomo, IN
Tel: 765-864-8360
Fax: 765-864-8387

Los Angeles

Mission Viejo, CA
Tel: 949-462-9523
Fax: 949-462-9608

Santa Clara

Santa Clara, CA
Tel: 408-961-6444
Fax: 408-961-6445

Toronto

Mississauga, Ontario,
Canada
Tel: 905-673-0699
Fax: 905-673-6509

ASIA/PACIFIC

Asia Pacific Office

Suites 3707-14, 37th Floor
Tower 6, The Gateway
Harbour City, Kowloon
Hong Kong
Tel: 852-2401-1200
Fax: 852-2401-3431

Australia - Sydney

Tel: 61-2-9868-6733
Fax: 61-2-9868-6755

China - Beijing

Tel: 86-10-8528-2100
Fax: 86-10-8528-2104

China - Chengdu

Tel: 86-28-8665-5511
Fax: 86-28-8665-7889

China - Hong Kong SAR

Tel: 852-2401-1200
Fax: 852-2401-3431

China - Nanjing

Tel: 86-25-8473-2460
Fax: 86-25-8473-2470

China - Qingdao

Tel: 86-532-8502-7355
Fax: 86-532-8502-7205

China - Shanghai

Tel: 86-21-5407-5533
Fax: 86-21-5407-5066

China - Shenyang

Tel: 86-24-2334-2829
Fax: 86-24-2334-2393

China - Shenzhen

Tel: 86-755-8203-2660
Fax: 86-755-8203-1760

China - Wuhan

Tel: 86-27-5980-5300
Fax: 86-27-5980-5118

China - Xiamen

Tel: 86-592-2388138
Fax: 86-592-2388130

China - Xian

Tel: 86-29-8833-7252
Fax: 86-29-8833-7256

China - Zhuhai

Tel: 86-756-3210040
Fax: 86-756-3210049

ASIA/PACIFIC

India - Bangalore

Tel: 91-80-4182-8400
Fax: 91-80-4182-8422

India - New Delhi

Tel: 91-11-4160-8631
Fax: 91-11-4160-8632

India - Pune

Tel: 91-20-2566-1512
Fax: 91-20-2566-1513

Japan - Yokohama

Tel: 81-45-471- 6166
Fax: 81-45-471-6122

Korea - Daegu

Tel: 82-53-744-4301
Fax: 82-53-744-4302

Korea - Seoul

Tel: 82-2-554-7200
Fax: 82-2-558-5932 or
82-2-558-5934

Malaysia - Kuala Lumpur

Tel: 60-3-6201-9857
Fax: 60-3-6201-9859

Malaysia - Penang

Tel: 60-4-227-8870
Fax: 60-4-227-4068

Philippines - Manila

Tel: 63-2-634-9065
Fax: 63-2-634-9069

Singapore

Tel: 65-6334-8870
Fax: 65-6334-8850

Taiwan - Hsin Chu

Tel: 886-3-572-9526
Fax: 886-3-572-6459

Taiwan - Kaohsiung

Tel: 886-7-536-4818
Fax: 886-7-536-4803

Taiwan - Taipei

Tel: 886-2-2500-6610
Fax: 886-2-2508-0102

Thailand - Bangkok

Tel: 66-2-694-1351
Fax: 66-2-694-1350

EUROPE

Austria - Wels

Tel: 43-7242-2244-39
Fax: 43-7242-2244-393

Denmark - Copenhagen

Tel: 45-4450-2828
Fax: 45-4485-2829

France - Paris

Tel: 33-1-69-53-63-20
Fax: 33-1-69-30-90-79

Germany - Munich

Tel: 49-89-627-144-0
Fax: 49-89-627-144-44

Italy - Milan

Tel: 39-0331-742611
Fax: 39-0331-466781

Netherlands - Drunen

Tel: 31-416-690399
Fax: 31-416-690340

Spain - Madrid

Tel: 34-91-708-08-90
Fax: 34-91-708-08-91

UK - Wokingham

Tel: 44-118-921-5869
Fax: 44-118-921-5820